

# Year 4 Science Pentecost Term: Electricity - Physics







## Key Vocabulary

Electricity	The flow of an electric current through a material.
Appliance	Equipment or a device designed to perform a particular job.
Circuit	A pathway that electricity can flow around,
Electrical conductor	A material that will allow electricity to flow through it.
Mains electricity	Electricity supplied through wires to a building.
Battery-powered	To make battery-powered appliances work, you need batteries - these could be rechargeable.

## Key Learning

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify if a lamp/switch will light in a simple series circuit, based on whether or not the lamp/switch is part of a complete loop with a battery.
- Recognise some common conductors and insulators, and associate metals with being good conductors.

## Components (Parts) of a Circuit

<p>Normally referred as a battery, scientifically this is a <b>cell</b>. It is the power supply for a circuit.</p> 	<p><b>Bulbs</b> light up in a complete circuit. They are placed in a bulb holder.</p> 	<p><b>Buzzers</b> make noise in a complete circuit.</p> 
<p><b>Wires</b> are used to connect the different components of a circuit together.</p> 	<p><b>Motors</b> produce movement in a complete circuit.</p> 	<p>A <b>switch</b> may be used to turn other components in a circuit on or off. They work as a 'break' in the circuit.</p> 

## Complete Circuits

Electricity can flow through complete circuits and the components will all work as they should.



## Incomplete Circuits

There is a break in the circuit that prevents the flow of electricity. The components will not work.

